

[dc circuits + capacitance] .quiz

1) ammeters and voltmeters

Consider an ideal voltmeter and an ideal ammeter, connected to a circuit like Fig. 1. The numerical values are  $E = 4.00 \text{ V}$ ,  $R_1 = 100 \Omega$ ,  $R_2 = 200 \Omega$ , and  $R_3 = 300 \Omega$ .

- a) Draw this circuit again, putting short circuits, i.e. simply wires, and/or open circuits instead of the meters.
- b) Find the current passing through  $R_2$ .
- c) Find the current passing through the ammeter and the voltage reading of the voltmeter.


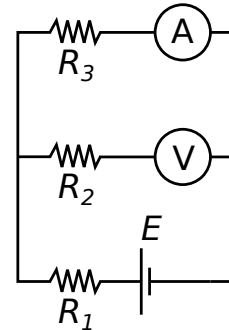


Figure 1: The circuit for the problem 2.

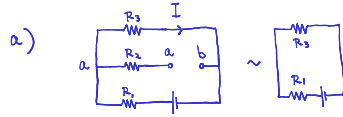

b) Zero.

c)  $I = \frac{E}{R_1 + R_3}$ ,  $V_a - V_b = R_3 I = \frac{R_3}{R_1 + R_3} E$ .

2) RC Circuits

Consider the RC circuit shown in fig. 1, where  $R_1 = 5.0 \text{ k}\Omega$ ,  $R_2 = 20 \text{ k}\Omega$ ,  $C_1 = C_2 = 4.7 \text{ mF}$ , and  $\mathcal{E} = 12 \text{ V}$ . The left switch is connected when  $0 < t < T$ , and the right switch is connected after that, i.e.  $t > T$ . Initially capacitors has no charge. For numerical values you can use  $T = 60 \text{ s}$ .

- a) Draw two circuits, one for  $0 < t < T$ , and the other one for  $t > T$ .
- b) Find  $V_{C_1}(t)$  when  $0 < t < T$ . What is the time constant?
- c) What happens right after the moment  $t = T$  when capacitors are connected in parallel?
- d) Find  $V_{C_1}(t)$  when  $t > T$ .
- e) Qualitatively plot  $V_{C_1}(t)$  versus time.



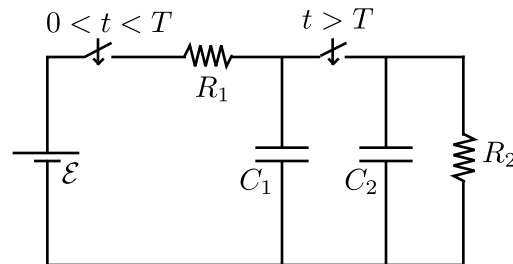


Figure 2: RC circuit, charging till  $t = T$  and discharging after that.

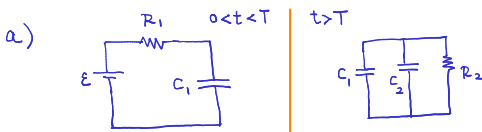

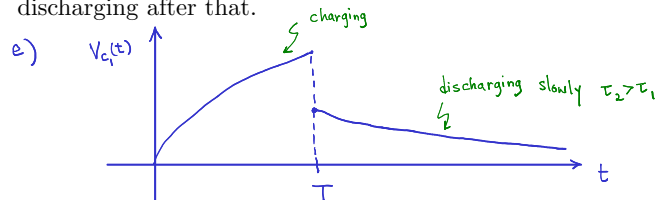b)  $0 < t < T$ :  $V_{C_1}(t) = \mathcal{E} [1 - e^{-t/\tau_1}]$ ,  $\tau = R_1 C_1$ .



c)  $V_{C_1} = V_{C_2} \rightarrow$  so they share total charge on  $C_1$  right before  $T$  between them so that  $\frac{q_1}{C_1} = \frac{q_2}{C_2}$ ,  $q_1 + q_2 = Q_{C_1}(T^-)$ . Here  $C_1 = C_2$  so each get half and  $V_{C_1}(T^+) = V_{C_2}(T^+) = \frac{1}{2} V_{C_1}(T^-) = \frac{1}{2} \mathcal{E} [1 - e^{-T/\tau_1}]$ .

d)  $t > T$ :  $V_{C_1}(t) = V_{C_1}(T^+) e^{-(t-T)/\tau_2}$ , It discharges through  $R_2$  with  $\tau_2 = R_2(C_1 + C_2)$ .