

[rlc circuits] .problems

1) Pieter van Musschenbroek connects his capacitor with capacitance $C = 2.2 \text{ mF}$ to a battery with emf $\mathcal{E} = 4.0 \text{ V}$ and a resistor $R = 20 \text{ k}\Omega$ in series. The capacitor was free of charge before connecting the circuit, at time $t = 0$.

- Calculate the time constant, τ .
- Draw a qualitative graph for capacitor voltage, $V_C(t)$, and resistor voltage, $V_R(t)$, versus time.
- How long it takes for the capacitor to get charged with $Q = 4.4 \text{ mC}$?

2) Felix Savary uses the same setup that we had in 'RLC Circuits' lab, part B, (R and L and C in series connected to a battery) and measures the current I (or voltage V_R) versus time as shown in fig. 1. He knows $R = 100\Omega$ and wants to find L and C . These are his measurements for two consecutive peaks:

$$\begin{aligned} t_1 &= 0.63 \text{ ms} \\ t_2 &= 1.13 \text{ ms} \\ I_1 &= 4.4 \text{ mA} \\ I_2 &= 2.8 \text{ mA} \end{aligned}$$

- Write an equation for L and C using t_1 and t_2 .
- Find the time constant, τ , using the values I_1 , I_2 , t_1 , t_2 .
- Find L and C , using previous parts.

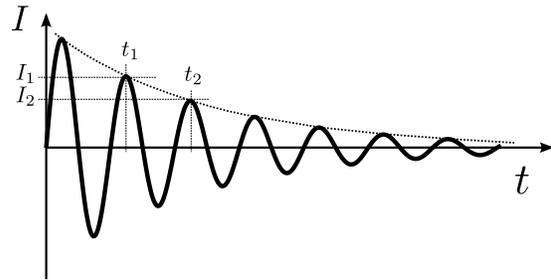


Figure 1: A series RLC circuit's current vs time.

3) Consider a series RLC circuit connected to a battery with voltage \mathcal{E} . The initial charge on the capacitor and the initial current are zero.

- Find $dI/dt(t = 0)$.
- If at a time $t = t_1$, the charge on the capacitor is $Q(t_1)$ and the current is changing with rate $dI/dt(t_1)$, determine $I(t_1)$.
- What are the values of Q, I, \dot{I} when $t \rightarrow \infty$?

4) Low-Pass, Band-Pass, & High-Pass Filters

Consider a series RLC circuit connected to an ac source, with voltage amplitude V and angular frequency ω . We want to understand the behavior of voltage across the capacitance, the resistance, and the inductance in different angular frequencies. If you use these voltages as an output, you can have a low-pass, band-pass, or high-pass filter, respectively.

- Find the total impedance of the circuit.
- Find V_C , V_R , and V_L , and show them in a phasor diagram.
- Now draw the graph of these voltages in terms of frequency. To do that first find their values at $\omega = 0$ and $\omega \rightarrow \infty$.
- For current or V_R there is a maximum point which is called resonance point. Find the frequency of this maximum point.