

tutorial #4 [electric circuits (cont.)] .quiz

1) Ewald Georg von Kleist connects two $\mathcal{E} = 12\text{ V}$ batteries with some $r = 100\ \Omega$ resistors and a capacitor on top with capacitance $C = 1.0\ \mu\text{F}$. He wants to find out how fast the capacitor charges, and at the end how much charge the capacitor would have. Ignore the capacitor for the first three parts.

- We name the currents on the left and right branches I_1 and I_2 . What is the current passing through the middle branch in terms of I_1 and I_2 ?
- Now that you know all the currents in terms of I_1 and I_2 , write two equations for voltages around the left and right loops. (Kirchhoff's loop rules)
- Solve these equations and find I_1 and I_2 . Now calculate $V_A - V_B$, which is the voltage the capacitor will have after a few time constants.
- Find the final charge on the capacitor.
- Now draw the same circuit, with the capacitor, but short circuit the batteries. Find the equivalent resistor from the capacitor's terminals.
- What is the time constant for charging the capacitor?

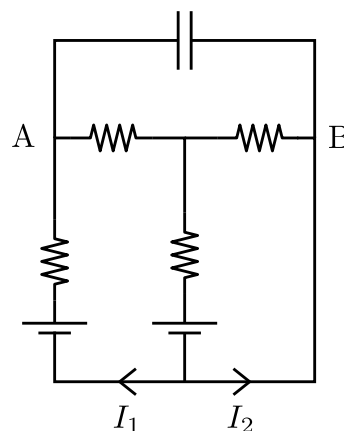


Figure 1: The circuit.

a) junction rule at X or Y : $I - I_1 - I_2 = 0 \rightarrow I = I_1 + I_2$.

b) loop 1: $\mathcal{E} + r(I_1 + I_2) + rI_1 + rI_1 - \mathcal{E} = 0$
 loop 2: $-rI_2 - r(I_1 + I_2) - \mathcal{E} = 0$

simplified:
$$\begin{cases} 3I_1 + I_2 = 0 & (i) \\ 2rI_2 + rI_1 = -\mathcal{E} & (ii) \end{cases}$$

c) (i) $\Rightarrow I_2 = -3I_1$ substituting in (ii)
 $\Rightarrow -6rI_1 + rI_1 = -\mathcal{E}$
 $\Rightarrow I_1 = \frac{\mathcal{E}}{5r} = 24\text{ mA}$
 and $I_2 = -3I_1 = -72\text{ mA}$




the negative sign means that the real current is in opposite direction.

$V_A - V_B = rI_1 - rI_2 = 100\ \Omega \times 24\text{ mA} - 100\ \Omega \times (-72\text{ mA}) = 9.6\text{ V}$.

d) $Q = CV = C(V_A - V_B) = 1\ \mu\text{F} \times 9.6\text{ V} = 9.6\ \mu\text{C}$.

e) $R_{eq} = r \parallel [r + (r \parallel r)]$
 $= \frac{3}{5}r = 60\ \Omega$

batteries short-circuited

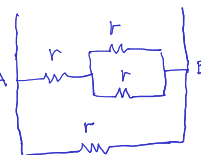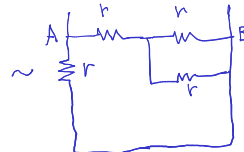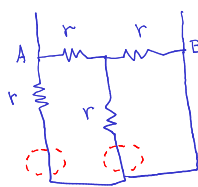

more familiar

f) $\tau = R_{eq} C = 60\ \Omega \times 1\ \mu\text{F} = 60\ \mu\text{s}$.