

Name:

1) CLASS(2)

Alessandro Volta connects a circuit as shown in fig. 1. $\mathcal{E} = 4 \text{ V}$, $R_1 = R_2 = 4 \Omega$, and $R_3 = R_4 = 8 \Omega$.

- a) Find V_{AC} .
- b) Find I_1 .
- c) Find V_{AB} .
- d) Find all other currents.

a) Any path from A to C will give us the voltage.
Here there is an easy path including only the battery.

$$V_{AC} = V_A - V_C = 4 \text{ V}.$$

$$b) R_{eq} = R_1 + (R_2 \parallel R_3 \parallel R_4) \\ = 4 \Omega + 2 \Omega = 6 \Omega.$$

$$\mathcal{E} - R_{eq} I_1 = 0 \rightarrow I_1 = \frac{\mathcal{E}}{R_{eq}} = \frac{2}{3} \text{ A}.$$

$$c) V_{AB} = R_1 I_1 = \frac{8}{3} \text{ V}.$$

$$d) V_{AC} = V_{AB} + V_{BC} \rightarrow V_{BC} = V_{AC} - V_{AB} = \frac{4}{3} \text{ V} \rightarrow \begin{cases} I_2 = V_{BC} / R_2 = \frac{1}{3} \text{ A} \\ I_3 = V_{BC} / R_3 = \frac{1}{6} \text{ A} \\ I_4 = V_{BC} / R_4 = \frac{1}{6} \text{ A} \end{cases}$$


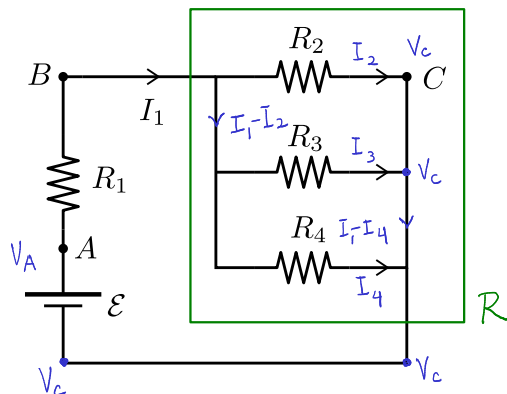


Figure 1: A circuit. $\frac{1}{R} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$
 $\rightarrow R = 2 \Omega.$

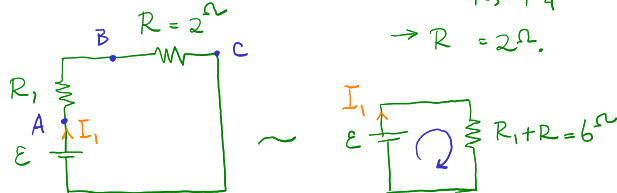

2) CLASS(2)

Ewald Georg von Kleist uses two $\mathcal{E} = 6 \text{ V}$ batteries and some 100Ω resistors to make a circuit as shown in fig. 2. Find the power dissipated in the R_4 resistor. [5 pts]

We need to find I_3 .

$$\begin{cases} \text{Junction (Node A)} & I_1 + I_2 + I_3 = 0 \quad (i) \\ \text{Loop 1} & \mathcal{E} - (R_1 + R_3)I_1 + R_2 I_2 - \mathcal{E} = 0 \rightarrow I_2 = I_1 \frac{R_1 + R_3}{R_2} \quad (ii) \\ \text{Loop 2} & \mathcal{E} - R_2 I_2 + R_4 I_3 = 0 \quad (iii) \end{cases}$$

$$(i), (ii) \rightarrow I_1 \left(\frac{R_1 + R_2 + R_3}{R_2} \right) + I_3 = 0 \quad (iv)$$

$$(iii), (iv), (ii) \rightarrow \mathcal{E} + \left[(R_1 + R_3) \frac{R_2}{R_1 + R_2 + R_3} + R_4 \right] I_3 = 0 \rightarrow I_3 = \frac{-\mathcal{E}}{\left[(R_1 + R_3) \frac{R_2}{R_1 + R_2 + R_3} + R_4 \right]} \\ = -36 \text{ mA}.$$

$$P_{R_4} = R_4 I_3^2 = 0.1296 \text{ W}.$$

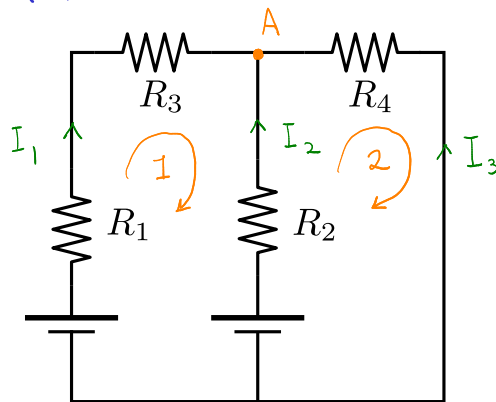


Figure 2: All resistors are equal.